

Physics ECAT Pre Engineering Chapter 16 Alternating Current Online Test

Sr	Questions	Answers Choice
1	When a transistor is used as a switch the circuit in which the current is to be switched OFF and ON, is connected between the	A. base and emitter B. collector and emitter C. base and collector D. any one of these
2	The basic circuit element in A.C. circuits are:	A. Resistor and capacitor B. Resistor and Inductor C. Capacitor only D. Both (B) and (C) E. None of these
3	For normal operation of transistor, the batteries	A. V_{CC} is of much lower value than V_{BB} B. V_{CC} is of much higher value than V_{BB} C. V_{CC} is equal to V_{BB} D. none of these
4	Which one of the following is correct?	A. $V_o = 1.414 V_{rms}$ B. $I_{rms} = 1.414 I_o$ C. $V_o = 10.70 V_{rms}$ D. Both a and b
5	Which of the following diode is used for the detection of light	A. photo diode B. light emitting diode C. photo voltaic cell D. all of them
6	The $R_1 = \infty$ and $R_2 = 0$, then the gain of non-inverting amplifier is	A. zero B. infinity C. one D. any one of these
7	The magnitude of alternative voltage V:	A. Always increase B. Always decrease C. Remains constant D. Does not remain constant E. None of these
8	An A.C varies as a function of	A. Current B. Voltage C. Time D. Charge
9	The total reactance of a series RLC circuit at resonance is	A. zero B. Equal to the resistance C. Infinity D. Capacitive
10	An A.C. voltmeter read 250 volts. The frequency of alternating is 50 Hz, the peak value of voltage is	A. 3525.0 volts B. 35.35 volts C. 353.5 volts D. 3.535 volts
11	The value of the potential difference across the depletion region for the case of germanium is	A. 0.3 V B. 0.5 V C. 0.7 V D. 0.9 V
12	A diode characteristic curve is a plot between	A. current and time B. voltage and time C. voltage and current D. forward voltage and reversed voltage
13	A signal is amplified at the output without any change of phase, if it is applied at the	A. inverting input B. non-inverting input C. at any of the input D. none of these
14		A. one of its instantaneous value B. Equal to its RMS value

14	Peak value of alternative current is:	C. The same as its peak-to-peak value D. Both (B) and (C) E. None of these
15	In half wave rectification	A. both halves of the input voltage is used B. only one half of the input voltage is used C. either of these D. none of these
16	The basic circuit elements of A.C circuit are	A. Resistor B. Inductor C. Capacitor D. All the three
17	Which of the following diodes can operate in the reverse biased condition	A. photo diode B. light emitting diode C. photo voltaic cell D. none of these
18	Due to the high value of the input resistance, practically, the value of the current which flows between the input terminals is	A. zero B. small C. large D. very large
19	The input resistance of the OP-AMP is the resistance between the	A. (-) input and output B. (+) input and output C. (-) and (+) inputs D. between any inputs
20	The power factor of resonant series circuit is	A. 1 B. 0 C. -1 D. 0.5
21	The entire wave form of sinusoidal voltage is actually a set of all the:	A. Positive maximum value + V_{max} and negative maximum value - V_{max} B. Positive maximum value + V_{max} and zero C. Zero and negative maximum value - V_{max} D. Any of these E. None of these
22	In frequency modulation (FM), the carrier waves amplitude	A. Remains constant B. Increase C. Decreases D. None of these
23	SI unit of impedance is	A. hertz B. henry C. ampere D. ohms
24	In an A.C circuit with resistor only, the current and voltage have a phase angle of	A. 90° B. 0° C. 180° D. none of these
25	Chock consumes externally small	A. Charge B. Current C. Power D. Potential
26	When the pn-junction is forward biased. the current flows through it is of the order of	A. milli-amperes B. amperes C. nano-amperes D. micro-amperes
27	The average of A.C. current and voltage over a complete cycle is	A. Maximum B. zero C. Neither zero nor maximum D. None of these
28	Average value of A.C voltage during one cycle is	A. 1 B. Zero C. Maximum D. Variable
		A. Instantaneous value B. RMS value

29	If we connected the ordinary DC ammeter to measure alternating current, it would measure its:	<p>D. RMS value</p> <p>C. Value averaged over a cycle</p> <p>D. Either (B) or (C)</p> <p>E. Either (A) or (C)</p>
30	When the p-n junction is forward biased its resistance is of the order of	<p>A. few mega ohms</p> <p>B. few kilo ohms</p> <p>C. few ohms</p> <p>D. few milli ohms</p>
31	When the pn-junction is connected reversed biased, its resistance is of the order of	<p>A. few ohms</p> <p>B. few kilo-ohms</p> <p>C. few mega-ohms</p> <p>D. few mili-ohms</p>
32	The alternative voltage of current is actually measured by:	<p>A. Its RMS value</p> <p>B. Square root of its mean square value</p> <p>C. Instantaneous value</p> <p>D. Peak value</p> <p>E. Both (A) and (B)</p>
33	A changing magnetic flux creates around itself	<p>A. An electromotive force</p> <p>B. An electric field (changing electric flux)</p> <p>C. Magnetic field</p> <p>D. None of the above</p>
34	A sinusoidally alternating voltage or current can be graphically represented by a:	<p>A. Vector</p> <p>B. Rotating vector</p> <p>C. Clockwise vector</p> <p>D. Anticlockwise voltage vector</p> <p>E. None of these</p>
35	The time interval during which the Voltage source changes its polarity once is known as:	<p>A. Time period T</p> <p>B. Half the time period</p> <p>C. Quarter the time period</p> <p>D. Two third of the time period</p> <p>E. None of these</p>
36	The phase at the positive peak of an A.C. cycle is:	<p>A. 0</p> <p>B. 90</p> <p>C. 180</p> <p>D. 0 and</p> <p>E. <</p>

language:EN-US;mso-bidi-language:AR-SA">۱/2 and 3
۱/2

37	The sum of positive and negative peak values is called:	A. Instantaneous value B. Peak value C. Rms value D. Peak-to peak-value E. None of these
38	In a transistor, if the central region is n-type, then this type of transistor is known as	A. n-p-n transistor B. p-n-p transistor C. either of these D. none of these
39	At higher frequency of the alternating current, the capacitive reactance X_C	A. Increases B. Decreases C. Remains the same D. Increases only when the voltage increases
40	If 250V is the RMS value of alternative voltage, then its peak value V_0 will be:	A. 353.5V B. 250V C. 175V D. zero E. 400V
41	During the positive half-cycle in the half-wave rectification, the diode	A. does not conduct B. conducts C. either of these D. neither of these
42	At resonance, the impedance of RLC series circuit is	A. Maximum B. Zero C. Minimum D. Determinate
43	Conversion of alternating current into direct current is called	A. amplification B. rectification C. conduction D. polarization
44	The emitter-base junction of a transistor is forward-biased and collector-base junction is reverse-biased. If the base current is increased, its	A. I_{CQ} will decrease B. V_{CEQ} will increase C. I_{CQ} will increase D. V_{CEQ} will increase
45	The highest value reached by the voltage or current:	A. In quarter cycle is called Instantaneous value B. In half cycle is called peak-to-peak value C. In one cycle is called peak value D. In half cycle is called Instantaneous value E. None of these
46	Most OP-AMP operates with	A. ± 6 V supply B. ± 10 V supply C. ± 12 V supply D. ± 24 V supply
47	An A.C. voltage is applied across the inductor. When the frequency of the voltage is increased, the current	A. Decreases B. Increases C. Does not change D. Momentarily goes to zero
48	A P-N junction or semiconductor diode cannot be used as	A. A rectifier B. Detector C. Oscillator D. An amplifier
49	In a normally biased n-p-n transistor, an electron current I_E flows from the	A. emitter into the base B. collector into the base C. base into collector D. none of these
50	Nowadays, Most of the electric energy is produced by the A.C. generators using:	A. Hydal water B. Geothermal energy C. Solar energy D. Biomass E. Wind energy

		E. Both (B) and (D)
51	When the pn-junction is in reversed biased, current flows through the junction due to the	A. majority carriers B. minority carriers C. either of them D. none of them
52	The value of output resistance of OP-AMOP is of the order of	A. few ohms B. few hundred ohms C. several kilo ohms D. several mega ohms
53	The phase angle of a series RLC circuit at resonance is	A. 180° B. 90° C. 0° D. None of these
54	Alternating current is produced by a voltage source which polarity:	A. Remains the same B. Reverse after period T C. Keeps on reversing with time D. Reverse after every time interval T/2 E. Both (C) and (D)
55	In free space, the speed of electromagnetic waves is	A. $3 \times 10^8 \text{ ms}^{-1}$ B. $3 \times 10^6 \text{ ms}^{-1}$ C. $4 \times 10^7 \text{ ms}^{-1}$ D. $3 \times 10^9 \text{ ms}^{-1}$
56	For a n-p-n transistor, the conventional current equation can be written as	A. $I_E = I_C + I_B$ B. $I_C = I_E - I_B$ C. $I_C = I_E + I_B$ D. $I_B = I_C + I_E$ E. $I_C = I_E$
57	If we connect a A.C. volt meter to read A.C. voltage, It would read its:	A. RMS value B. Instantaneous value C. Valued average over a cycle D. Zero E. Both (B) and (C)
58	In which of the following components, pn-junction is used	A. light emitting diode B. photo diode C. photo voltaic cell D. all of these
59	In which of the following diodes when an electron combines with a hole during the forward biasing, photon of visible light is emitted.	A. photo diode B. light emitting diode C. photo voltaic cell D. all of them
60	Electromagnetic waves transmit energy equal to	A. $\frac{1}{2} mv^2$ B. $m\omega^2 c^2$ C. hf/c D. hf
61	In RLC series circuit, resonance occurs when	A. $X_L > X_C$ B. $X_L < X_C$ C. $X_L = X_C$ D. None of these
62	A resonance curve for RLC series circuit is a plot of frequency versus	A. Voltage B. Current C. Impedance D. Reactance
63	The closed loop gain of the inverting amplifier is written as	A. $G = R_2/R_1$ B. $G = 1 + R_2/R_1$ C. $G = -R_2/R_1$ D. $G = 1 - R_2/R_1$
64	When electrons in the transmitting antenna vibrate 94000 time per second, they produce radiowaves having frequency	A. 9.4 kHz B. 940 kHz C. 94 kHz D. None of these

		D. none of these
65	A p-n junction is formed when a crystal of silicon is grown in such a way that its one half is doped with trivalent impurity and the other half with an impurity from	A. 2nd group B. fourth group C. fifth group D. sixth group
66	The open loop gain of OP-AMP is of the order of	A. 10^2 B. 10^3 C. 10^4 D. 10^5
67	The device which allows only the flow of an A.C. through a circuit is	A. Capacitor B. Inductor C. D.C. motor D. Battery
68	The output voltage of half wave rectification is in the form of	A. a smooth curve B. a smooth wave C. pulses D. all of the above
69	In n-p-n transistor, emitter base junction is kept	A. reversed B. forward biased C. may be reversed or may be forward biased D. none of these
70	Alternating current can induce voltage because it has a	A. High peak value B. Varying magnetic field C. Stronger field than direct current D. Constant magnetic field
71	Transmitting antenna emits	A. Magnetic waves B. Electric waves C. Electromagnetic waves D. Sound waves
72	Alternating current can be transmitted:	A. To long distance B. At very high cost C. At very low cost D. Both (A) and (C) E. Both (A) and (B)
73	Which one of the following Electro-magnetic waves have the highest frequency and shortest wave-length	A. X-rays B. Ultraviolet rays C. γ -rays D. Cosmic rays
74	In a transistor, if the central region is p-type then this type of transistor is known as	A. p-n-p transistor B. n-p-n transistor C. either of these D. none of these
75	A digital system deals with quantities or variables which have	A. only one state B. only two discrete states C. three discrete states D. four discrete states
76	The Instantaneous value of alternative current may be:	A. The same as its RMS value B. Greater than its RMS value C. The same as its peak value D. Any of these E. None of these
77	Which of the following diode is used to derive the current in external circuit when light is incident in the circuit	A. photo diode B. light emitting diode C. photo voltaic cell D. none of these
78	During the negative half-cycle of the half-wave rectification, the diode	A. does not conduct B. conducts C. either of these D. none of these
79	The waveform of alternating voltage is a:	A. Square B. Rectangular C. Saw-tooth D. Sinusoidal E. None of these
80	When either L or C is increased, the resonant frequency of the RLC series circuit	A. Increases B. Decreases C. Remains the same D. Becomes zero
81	When the emitter-base junction of a transistor is reverse biased, collector current	A. Reverses B. Increases C. Decreases D. Stops

82	If the value of C in a series RLC circuit is increased, the resonant frequency	A. Is not affected B. Increase C. Remains the same D. Decreases
83	The most common source of alternating voltage is:	A. Motor B. Transformer C. AC generator D. Both (A) and (C) E. Both (A) and (B)
84	OP-AMP has the following input terminals	A. one B. two C. three D. four
85	Which of the following has a great concentration of impurity	A. base B. emitter C. collector D. none of these
86	The length of rotating vector (on a certain scale) represents the:	A. Peak value of alternating quantity B. RMS value of alternating quantity C. Instantaneous value of alternating quantity D. Either (B) or (C) E. Either (A) or (B)
87	The circuit which is used to smooth the output voltage of the full-wave rectification is known as	A. transformer B. rectifier C. filter D. none of these
88	The r.m.s. value of alternating current is equal to its maximum value at angle of	A. 60° B. 45° C. 30° D. 90°
89	Unless stated otherwise, when we speak of A.C. meter reading, we usually mean:	A. Peak value B. RMS value C. Instantaneous value D. Peak-to-peak value E. Both (A) and (C)
90	At resonance, the phase angle for RLC series resonance circuit equals	A. 0° B. 90° C. 180° D. 270°
91	The value of the input resistance of OP-AMP is of the order of	A. few ohms B. few hundred ohms C. several kilo ohms D. several mega ohms
92	The value of current gain of n-p-n transistor is of the order of	A. tens B. hundreds C. thousands D. ten thousands
93	During each cycle, alternating voltage reaches a peak value	A. One time B. Two times C. Four times D. A number of times depending on the frequency
94	In series RC circuit when $R = X_C$, then the phase angle is	A. 0° B. 90°

94	In series RC circuit when $X_C = R$, then the phase angle is	<p>C. 70°</p> <p>D. 45°</p>
95	The basic circuit element in D.C. circuit is:	<p>A. A capacitor</p> <p>B. A resistor</p> <p>C. An inductor</p> <p>D. Both (A) and (C)</p> <p>E. Both (A) and (B)</p>
96	Mathematical manipulation of the two quantized states can be best carried if they are represented by	<p>A. high - low</p> <p>B. yes - no</p> <p>C. on - off</p> <p>D. 0 - 1</p>
97	For the normal operation of the transistor, its	<p>A. emitter-base and collector base junctions are forward biased</p> <p>B. emitter-base junction is reversed biased and collector base junction is forward biased</p> <p>C. emitter-base junction is forward biased and collector-base junction is reverse biased</p> <p>D. any one of these</p>
98	To design a resonant circuit of frequency 100 KHz with an inductor of inductance 5 mH, we need a capacitor of capacitance	<p>A. 5.07 pF</p> <p>B. 50 pF</p> <p>C. 0.507 pF</p> <p>D. 507 pF</p>
99	In a transistor, the central region is called	<p>A. collector</p> <p>B. emitter</p> <p>C. base</p> <p>D. none of them</p>
100	In describing functions of digital systems, a closed switch will be shown as	<p>A. 0</p> <p>B. 1</p> <p>C. low</p> <p>D. any one of these</p>
101	The closed loop gain of the non-inverting amplifier is given by	<p>A. $G = \frac{R_2}{R_1}$</p> <p>B. $G = -\frac{R_2}{R_1}$</p> <p>C. $G = 1 + \frac{R_2}{R_1}$</p> <p>D. $G = 1 + \frac{R_2}{R_1}$</p>
102	The bridge circuit of full wave rectification uses	<p>A. one diode</p> <p>B. two diode</p> <p>C. three diode</p> <p>D. four diode</p>
103	The impedance of RLC series resonance circuit at resonant frequency is	<p>A. Greater than R</p> <p>B. Equal to R</p> <p>C. Less than R</p> <p>D. None of these</p>
104	The RMS value of alternating current is:	<p>A. 0.7 times at the peak value</p> <p>B. 0.5 times the peak value</p> <p>C. 0.7 times the Instantaneous value</p> <p>D. Equal to maximum voltage</p> <p>E. None of these</p>
105	The amplifier which is used to perform mathematical operations electronically is known as	<p>A. calculator</p> <p>B. OP-AMP</p> <p>C. computer</p> <p>D. any one of them</p>
106	The wave form of alternating voltage is the graph between:	<p>A. Voltage across X-axis and time across y-axis</p> <p>B. Current and time</p> <p>C. Voltage along y-axis and time along x-axis</p> <p>D. Voltage and current</p> <p>E. Either (B) or (D)</p>
107	At resonance frequency the impedance of parallel resonance circuit is	<p>A. Maximum</p> <p>B. Minimum</p> <p>C. Zero</p> <p>D. None of the above</p>
108	Which one of the following waves belongs to electromagnetic spectrum	<p>A. Radio and TV waves</p> <p>B. Radar waves</p> <p>C. Micro waves</p> <p>D. All of these</p>

109

A signal appears after amplification, at the output terminal with a phase shift of 180° , if it is applied at

D. All of them

A. inverting input

B. non-inverting input

C. any one of the input terminal

D. none of them