

MDCAT Physics Chapter 10 Current Electricity MCQ's Test

Sr	Questions	Answers Choice
1	Electric current is defined as:	A. Flow of charges through conductor B. Rate of flow of charges through conductor C. Flow of electrons D. Flow of protons
2	A 100W, 220V bulb is operated on a 110V line, the power consumed is:	A. 25W B. 75W C. 50W D. 100W
3	The rate at which the battery is supplying the electrical energy is the:	A. Power output B. Electrical power C. Power input D. Both A and C
4	A steady current is flowing in a conductor of non-uniform cross-section. The charge passing through any cross-section per unit time is	A. Directly proportional to the area of cross-section B. Inversely proportional to the area of cross-section C. Proportional to square of the area of cross-section D. Independent of the area of cross-section
5	When resistances are connected in Parallel, the effective resistance will be	A. Product of the reciprocals of the individual resistances B. Product of the individual resistances C. Sum of the reciprocals of the individual resistances D. Sum of the individual resistances
6	A total charge of 100C flows through 12W bulb in a time of 50 second. Which is the potential difference across the bulb during this time?	A. 0.12V B. 6.0V C. 2.0V D. 24V
7	A piece of Aluminium (Al) and a piece of Germanium (Ge) are cooled T1 K to T2 K. The resistance of:	A. Each of them increases B. Each of them decreases C. Al increases and Ge decreases D. Al decreases and that of Ge increases
8	An electric room radiator, which operates at 50V has resistance of 50 Ω. Power of the radiator is approximately:	A. 100W B. 50W C. 450W D. 1000W
9	The emf of a cell of negligible internal resistance is 2V. It is connected to the series combination of 1Ω, 2Ω, 3Ω, 4Ω resistance. The potential difference across 3Ω resistance will be in volt:	A. 0.6 B. 2/3 C. 3 D. 6
10	Two wires of same material have lengths L and 2L and cross-sectional area 4A and A respectively. the ratio of their specific resistance would be:	A. 1: 1 B. 1: 8 C. 8: 1 D. 1: 2
11	Which of the Following bulb will glow Brightest?	A. 100W B. 200W C. 300W D. 400W
12	The 'emf' is always even when no current is drawn through the battery of the cell:	A. Zero B. Present C. Absent D. Maximum
13	The specific resistance of a wire varies with its:	A. Length B. Cross-section C. Mass D. Material

14	A charge of 90C passes through a wire in 1 hour and 15 minutes. What is the current in the wire?	A. 10mA B. 20mA C. 15mA D. 25mA
15	Resistance of 60 watt bulbs in 120V line is:	A. 20 ohms B. 240 ohms C. 0.15 ohms D. 180 ohms
16	If a source of emf is traversed from positive to negative the potential change will be:	A. Positive B. Negative C. Zero D. Constant
17	A cell of negligible resistance and e.m.f 2 V is connected across a series combination of 2,3 and 5 ohms. The p.d. across the 3 Ω resistor is	A. 0.6 V B. 1/3 V C. 2/3 V D. 4/3 V
18	There are two electric bulbs of 40 W and 100 W. They are first connected in series and then in parallel across a source:	A. 40W bulb will be brighter in series and 100W in parallel B. 100W bulb will be brighter in series and 40W in parallel C. 40W bulb will be brighter in both the cases D. 100W bulb will be brighter in both the cases
19	When the length and area of cross-section both are doubled, then its resistance:	A. Will become half B. Will remain the same C. Will be doubled D. Will become four times
20	The product of resistance and conductance of a resistor is equal to:	A. 1 B. Conductivity C. Resistivity D. Zero