

## General Science 6th Class English Medium Chapter 9 Online Test

Sr	Questions	Answers Choice
1	A device used to open or close an electric circuit.	A. Switch B. Wire C. Battery D. Bulb
2	The type of circuit used in domestic wiring.	A. Series B. Parallel C. Open D. Short
3	The type of circuit used in domestic wiring.	A. Open B. Short C. Series D. Parallel
4	A circuit that provides multiple paths to the current to flow.	A. Series B. Open C. Short D. Parallel
5	A device that stores chemical energy and converts it into electric energy when connected in a circuit.	A. Cell B. Bulb C. Metallic wire D. Electric switch
6	A positively charged particle.	A. Electron B. Proton C. Neutron D. Atom