

## ECAT Physics Chapter 16 Alternating Current Online Test

Sr	Questions	Answers Choice
1	Electromagnetic waves transmit energy equal to	A. 1/2 mv <sup>2</sup> B. m <sub>o</sub> c <sup>2</sup> C. hf/c D. hf
2	Due to the high value of the input resistance, practically, the value of the current which flows between the input terminals is	A. zero B. small C. large D. very large
3	In n-p-n transistor, emitter base junction is kept	A. reversed B. forward biased C. may be reversed or may be forward biased D. none of these
4	A diode characteristic curve is a plot between	A. current and time B. voltage and time C. voltage and current D. forward voltage and reversed voltage
5	For the normal operation of the transistor, its	A. emitter-base and collector base junctions are forward biased B. emitter-base junction is reversed biased and collector base junction is forward biased C. emitter-base junction is forward biased and collector-base junction is reverse biased D. any one of these
6	The time interval during which the Voltage source changes its polarity once is known as:	A. Time period T B. Half the time period C. Quarter the time period D. Two third of the time period E. None of these
7	Which of the following diode is used for the detection of light	A. photo diode B. light emitting diode C. photo voltaic cell D. all of them
8	When the pn-junction is forward biased. the current flows through it is of the order of	A. mili-amperes B. amperes C. nano-amperes D. micro-amperes
9	During each cycle, alternating voltage reaches a peak value	A. One time B. Two times C. Four times D. A number of times depending on the frequency
10	In which of the following diodes when an electron combines with a hole during the forward biasing, photon of visible light is emitted.	A. photo diode B. light emitting diode C. photo voltaic cell D. all of them
11	When either L or C is increased, the resonant frequency of the RLC series circuit	A. Increases B. Decreases C. Remains the same D. Becomes zero
12	The closed loop gain of the non-inverting amplifier is given by	A. G = R <sub>2</sub> /R <sub>1</sub> B. G = - R <sub>2</sub> /R <sub>1</sub> C. G = 1 - R <sub>2</sub> /R <sub>1</sub> D. G = 1 + T <sub>2</sub> /R <sub>1</sub>
13	In a transistor. if the central region is p-type then this type of transistor is known as	A. p-n-p transistor B. n-p-n transistor

		C. either of these D. none of these
14	Alternating current is produced by a voltage source which polarity:	A. Remains the same B. Reverse after period T C. Keeps on reversing with time D. Reverse after every time interval T/2 E. Both (C) and (D)
15	At resonance frequency the impedance of parallel resonance circuit is	A. Maximum B. Minimum C. Zero D. None of the above
16	A resonance curve for RLC series circuit is a plot of frequency versus	A. Voltage B. Current C. Impedance D. Reactance
17	The waveform of alternating voltage is a:	A. Square B. Rectangular C. Saw-tooth D. Sinusoidal E. None of these
18	The total reactance of a series RLC circuit at resonance is	A. zero B. Equal to the resistance C. Infinity D. Capacitive
19	The basic circuit elements of A.C circuit are	A. Resistor B. Inductor C. Capacitor D. All the three
20	Which one of the following is correct?	A. V <sub>o</sub> = 1.414 V <sub>rms</sub> B. I <sub>ams</sub> = 1.414 I <sub>o</sub> C. VO = 10.70 Vrms D. Both a and b