

## Physics FSC Part 2 Chapter 13 Online MCQ's Test

Sr	Questions	Answers Choice
1	An ideal current source shall have resistance	<p>A. Zero</p> <p>B. Finite but not zero</p> <p>C. Infinite</p> <p>D. Depend upon requirement</p>
2	Tolerance of "Gold" band.	<p>A. <math>\pm 10\%</math></p> <p>B. <math>\pm 5\%</math></p> <p>C. <math>\pm 15\%</math></p> <p>D. <math>\pm 20\%</math></p>
3	The unit of temperature co efficient of resistivity is.	<p>A. Ohm -m</p> <p>B. K-1</p> <p>C. K</p> <p>D. Ohm</p>
4	e.m.f is the conversion of ----- energy into electrical energy	<p>A. Chemical</p> <p>B. Solar</p> <p>C. Light</p> <p>D. None of these</p>
5	Calculate current in 2 $2R/4\Omega$ resistor.	<p>A. 1 A</p> <p>B. <math>2R/4\Omega</math></p> <p>C. <math>R/3\Omega</math></p> <p>D. <math>2R/3\Omega</math></p>
6	A certain wire has a resistance R, the resistivity of an other wire of an identical material with the first, except for twice its diameter is.	<p>A. <math>1/4 R</math></p> <p>B. <math>4R</math></p> <p>C. <math>2R</math></p> <p>D. Same as R</p>
7	The powers of two electric bulbs are 100w and 200w. Which are connected to power supply of 220 V. The ratio of resistance of their filament will be:	<p>A. <math>1/2</math></p> <p>B. <math>2/1</math></p> <p>C. <math>3/4</math></p> <p>D. <math>4/3</math></p>
8	When a wire is stretched and its radius becomes $r/2$ , then its resistance will be	<p>A. <math>16 R</math></p> <p>B. <math>4 R</math></p> <p>C. <math>2R</math></p> <p>D. 0</p>
9	The resistivity of two wires is $\rho_1$ and $\rho_2$ which are connected in series. If there dimentions are same then the equivalent resistivity of the combination will be:	<p>A. <math>(\rho_1 + \rho_2)</math></p> <p>B. <math>\frac{\rho_1 + \rho_2}{2}</math></p> <p>C. <math>\frac{\rho_1 \rho_2}{\rho_1 + \rho_2}</math></p> <p>D. <math>\frac{\rho_1 \rho_2}{\rho_1 - \rho_2}</math></p>

