

## Physics FSC Part 2 Chapter 16 Online MCQ's Test

Sr	Questions	Answers Choice
1	In RLC series circuit at resonance the phase difference between capacitor and inductor reactance is.	A. $90^\circ$ B. $270^\circ$ C. $0^\circ$ D. $180^\circ$
2	The device which allows only the continuous flow of AC through it is.	A. Inductor B. Battery C. Thermistor D. Capacitor
3	100 micro F capacitor is connects to an AC voltage 24 V and frequency 50 Hz. The reactance of the capacitor is.	A. 30.8 Ohm B. 31.8 Ohm C. 34.8 Ohm D. 40 Ohm
4	The value of capacitive reactance is given by	A. $X_C = VI$ B. $X_C = 1/\omega C$ or $X_C = \omega C$ C. $X_C = 1/\omega C$ or $X_C = \omega C$ D. All of above
5	At high frequency the value of reactance of capacitor will be.	A. Small B. Zero C. Large D. Infinite
6	$X_L$ is low for low frequency F and $X_C$ is.	A. Zero B. Low C. High D. Same as H
7	Power dissipated in a pure inductor is.	A. Large B. Small C. Infinite D. Zero
8	The power factor of RL series circuit is.	A. 0 B. 1 C. Less than 1 D. More than one
9	The highest value reached by the voltage or current is one cycle is called:	A. Peak to peak value B. Peak value C. Instantaneous value D. Root mean square value
10	The peak value of alternating current is $5\sqrt{2}$ A. The mean square value of current will be:	A. 5 A B. 2.5 A C. $5\sqrt{2}$ A D. $5\sqrt{2}$ A
11	In purely resistive A.C circuit, instantaneous value of voltage and current:	A. Current lags behind voltage by $\pi/2$ B. Current leads voltage by $\pi/2$ C. Both are in Phase D. Voltage leads current by $\pi/2$
12	The natural frequency of L.C circuit is equal to	
13	SI unit of reactance is.	A. Ohm B. Mho C. Farad D. Henry
14	A resistance frequency the impedance of RLC parallel circuit is.	A. Zero B. Infinite C. Maximum D. Minimum
15	The peak value of alternating current is $5\sqrt{2}$ A. The mean square value of current will be:	A. 5 A B. 2.5 A C. $5\sqrt{2}$ A

font-family: arial, sans-serif; font-size: 16px;">"  $\sqrt{2}A$

D.  $5\sqrt{2}$

---

16 Radio frequency choke is

A. Iron cored  
B. Air Cored  
C. Air as well as iron cored  
D. None of these

---

17 An inductor of 1 henry inductance has a reactance 500 ohms, then the frequency required is approximately

A. 50 Hz  
B. 100 Hz  
C. 80 Hz  
D. 120 Hz

---

18 The peak to peak value of alternating voltage is

A.  $2V\sqrt{2}$   
B.  $V\sqrt{2}$   
D. None of these

---

19 Choke consumes extremely small

A. Current  
B. Charge  
C. Power  
D. Potential

---

20 In an LRC circuit, the capacitance is made one-fourth, when in resonance. Then what should be change in inductance, so that the circuit remain in resonance?

A. 4 times  
B. 1/4 times  
C. 8 times  
D. 2 times