

## Physics FSC Part 2 Chapter 16 Online MCQ's Test

Sr	Questions	Answers Choice
1	An A.C. voltmeter reads 220 V, its peak value will be	A. 225 V B. 240 V <b>C. 311.12 V</b> D. 300 V
2	In choke coil the resistance $X_L$ an resistance R are:	A. $X_{sub>L</sub>}=R$ B. $X_{sub>L</sub>}<lt;&lt;R$ <b>C. <math>X_{sub&gt;L&lt;/sub&gt;}&gt;gt;&amp;gt;R</math></b> D. $X_{sub>L</sub>}=<span style="color: rgb(34, 34, 34); font-family: arial, sans-serif; font-size: 16px;">∞</span>$
3	The highest value reached by the voltage or current in one cycle is called.	A. Peak or peak value <b>B. Peak value</b> C. Instantaneous value D. Root mean square value
4	The electromagnetic spectrum contains	A. Radio waves B. X-rays C. Microwaves <b>D. All of these</b>
5	The device which allows only the continuous flow of AC through it is.	A. Inductor B. Battery C. Thermistor <b>D. Capacitor</b>
6	At high frequency the value of reactance of capacitor will be.	A. Small B. Zero C. Large <b>D. Infinite</b>
7	An electromagnetic wave goes from air to glass which of the following does not change?	A. Radio waves B. X-rays C. Ultra violet radiation <b>D. Ultra sound waves</b>
8	If $V_{rms}$ be the root mean square value of emf then its peak to peak value is given by	<b>A. <math>2\pi f L</math></b> B. $1/2\pi f L$ C. $2\pi f L$ D. $f L/2\pi$
9	$X_L =$	<b>A. Inductor</b> B. Resistor C. Motor D. All of these
10	Which consumes small power.	<b>A. 2</b> B. $V_{sub>0</sub>}$ C. $V_{sub>0</sub>}^2$ D. $V_{sub>0</sub>}^2/2$
11	The peak to peak value of alternating voltage is	<b>A. <math>2V_{sub&gt;0&lt;/sub&gt;}</math></b> B. $V_{sub>0</sub>}$ C. None of these
12	The peak value of A.C source is 20 A, then its rms value will be.	<b>A. 14.1 A</b> B. 10 A C. 20 A D. 28.2 A
13	The phase difference between the current and voltage at resonance is:	<b>A. 0</b> B. $\pi$ C. $-\pi$ D. $\pi/2$
14	In case of capacitor, the unit of reactance is	<b>A. Farad</b> <b>B. Ohm</b> C. Newton D. All of these

---

15 The circuit in which current and voltage are in phase, the power factor is:  
A. Zero  
B. 1  
C. -1  
D. 2

---

16 An alternating voltage is given by  $20 \sin 157 t$ . The frequency of alternating voltage is:  
A. 50 Hz  
B. 25 Hz  
C. 100 Hz  
D. 75 Hz

---

17 The natural frequency of L.C circuit is equal to

---

18 The reactance of inductor depends upon  
A. L  
B. Constant  
C. Infinite  
D. All of the above

---

19 The velocity of an oscillating charge as it moves to and fro along a wire is.  
A. Changing  
B. Constant  
C. Infinite  
D. zero

---

20 In three phase A.C. generator the phase difference between each pair of coil is.  
A.  $45^\circ$   
B.  $90^\circ$   
C.  $120^\circ$   
D.  $60^\circ$

---