

Physics ICS Part 2 Chapter 16 Online MCQ's Test

| Sr | Questions | Answers Choice |
|----|--|--|
| 1 | The wave form of alternating voltage is a | A. Cotangent curve B. Cosine curve C. Sine curve D. Tangent curve |
| 2 | The condition of resonance is: | A. $XL = 1/2 Xc$ B. $X_L _L = X_c$ C. $X_c = 4_x2</sub>$ D. None of above |
| 3 | X_L is low for low frequency F but Xc is. | A. Zero B. Low C. High D. Same is H |
| 4 | $X_L =$ | A. $2\pi f L$ B. $1/2\pi f L$ C. $2\pi f L$ D. $f L/2\pi$ |
| 5 | An A.C. voltmeter reads 220 V, its peak value will be | A. 225 V B. 240 V C. 311.12 V D. 300 V |
| 6 | The flow of D.C current is opposed by | A. Resistor B. Induction C. Capacitor D. All of these |
| 7 | The circuit in which current and voltage are in phase, the power factor is: | A. Zero B. 1 C. -1 D. 2 |
| 8 | An inductor of 1 henry inductance has a reactance 500 ohms, then the frequency required is approximately | A. 50 Hz B. 100 Hz C. 80 Hz D. 120 Hz |
| 9 | The combined effect of resistance and reactance in circuit is called: | A. Impedance B. Inductance C. Capacitance D. None of above |
| 10 | In pure capacitor A.C. circuit, the current I and charge q are. | A. In phase B. Out of phase C. Parallel to each other D. None of above |
| 11 | $Xc =$ | A. $1/2\pi f C$ B. $2\pi f C$ C. $2\pi/f C$ D. $f C/2\pi$ |
| 12 | The device which allows only the continuous flow of AC through it is. | A. Inductor B. Battery C. Thermistor D. Capacitor |
| 13 | The unit of impedance is. | A. Henry B. Hertz C. Ampere D. Ohm |
| 14 | The internal resistance of a capacitor is called: | A. Impedance B. Resistance C. Reactance D. Conductance |
| 15 | Impedance is denoted by: | A. A B. Z C. P D. Q |

| | | |
|----|---|---|
| 16 | In an LRC circuit, the capacitance is made one-fourth, when an resonance . Then what should be change in inductance, so that the circuit remain in resonance? | A. 4 times B. 1/4 times C. 8 times D. 2 times |
| 17 | In choke coil the resistance X_L an resistance R are: | A. $X_{sub}L</sub>=R$ B. $X_{sub}L</sub><lt;<R$ C. $X_{sub}L</sub>>gt;R$ D. $X_{sub}L</sub>=∞$ |
| 18 | In purely resistive A.C circuit, instantaneous value of voltage and current: | A. Current lags behind voltage B. Current leads voltage by $π/2$ C. Both are in Phase D. Voltage leads current by $π/2$ |
| 19 | Power dissipation in A.C circuit is expressed as: | A. $P = I_{sub}rms _x V_{sub}rms _{Sinθ}$ B. $I_{sub}V_{sub}Cosθ$ C. $I_{sub}rms _x V_{sub}rms _{Cosθ}$ D. $I_{sub}rms _x V_{sub}rms _{Sin2θ}$ |
| 20 | In frequency modulation, the amplitude of carrier waves is | A. Increases B. Remains constant C. Decreases D. None of these |