

Physics ICS Part 2 Chapter 16 Online MCQ's Test

Sr	Questions	Answers Choice
1	The unit of impedance is	A. Farad B. Henry C. Tesla D. Ohm
2	SI unit of reactance is.	A. Ohm B. Mho C. Farad D. Henry
3	X_L is low for low frequency F but X_C is.	A. Zero B. Low C. High D. Same is H
4	In modulation, low frequency signal is known as	A. Carrier wave B. fluctuated signal C. Modulated carrier signal D. Modulation signal
5	An inductor of 1 henry inductance has a reactance 500 ohms, then the frequency required is approximately	A. 50 Hz B. 100 Hz C. 80 Hz D. 120 Hz
6	The peak to peak value of alternating voltage is	A. $2V_m$ B. V_m C. V_m D. None of these
7	In three phase voltage across any two lines is about.	A. 220 V B. 230 V C. 400 V D. 430 V
8	The basic circuit element in A.C. circuit which controls current.	A. Resistor only B. Capacitor only C. Inductor only D. All of these
9	Choke consumes extremely small	A. Current B. Charge C. Power D. Potential
10	Power dissipated in a pure inductor is.	A. Large B. Small C. Infinite D. Zero
11	Resistance of choke is	A. zero B. Large C. Very small D. Infinite
12	In case of A.C. through resistor V and I are	A. At 0° with each other B. At 180° with each other C. At 90° with each other D. At 270° with each other
13	An A.C. voltmeter reads 220 V, its peak value will be	A. 225 V B. 240 V C. 311.12 V D. 300 V
14	The effective value of any sinusoidal alternating current or voltage is	D. None of the above
15	In AC system we generate sine wave form because:	A. It can be easily draw B. It produces least disturbance in electrical circuits C. It is nature standard D. Other waves cannot be produced easily

16	In an LRC circuit, the capacitance is made one-fourth, when at resonance. Then what should be change in inductance, so that the circuit remain in resonance?	<p>A. 4 times</p> <p>B. 1/4 times</p> <p>C. 8 times</p> <p>D. 2 times</p>
17	The velocity of an oscillating charge as it moves to and fro along a wire is.	<p>A. Changing</p> <p>B. Constant</p> <p>C. Infinite</p> <p>D. zero</p>
18	The reactance of inductor depends upon	<p>A. L</p> <p>D. All of the above</p>
19	The reactance is the ratio of	<p>A. V_{rms}/I_{rms}</p> <p>B. $V_{rms} \times I_{rms}$</p> <p>C. I_{rms}/V_{rms}</p> <p>D. $V_{max} \times V_{rms}$</p>
20	In three phase A.C. generator the phase difference between each pair of coil is.	<p>A. 45°</p> <p>B. 90°</p> <p>C. 120°</p> <p>D. 60°</p>