

Computer Science (New Book) - 9thClass Computer Science English Medium Chapter 3 Preparation

Q1. Define Digital Logic.

Ans 1: Digital logic is the basis of all digital systems. This is the technique we use to process digital information in the form of binary numbers.

Q2. Differentiate between Half and Full adder.

Ans 1: A half adder is digital circuit used to compute the addition of two single-bit binary numbers. A full adder is a more complex circuit that adds three single bit numbers two main bits and a carry bit from a previous addition.

Q3. Define K-map

Ans 1: A Karnaugh map is a graphic aid that is employed in simplification of Boolean expressions and minimizing logic function without the need for complex algebraic operations.

Q4. Define Digital Signals

Ans 1: Digital signals are the signals which have only two values that are in the form '0' and '1' these are utilized in digital electronics and computing systems. Analog to digital converter and digital to analog converter are important operations in today's technological development, enabling the transmission and control of signals.

Q5. Explain the word propagation delay in terms of digital logic gates.

Ans 1: Propagation delay is the time it takes for an input change to result in an output change in a logic gate. It influences the overall performance of digital circuits.

Q6. What is Boolean Algebra.

Ans 1: Boolean algebra is a sub discipline of mathematics based on operations involving binary variables.

Q7. What do you know about AND operation.

Ans 1: In the case of AND operation the output is 1 only when both input values are 1. Otherwise, the output is 0

Q8. What is multiplexer and how does it work in digital circuits.

Ans 1: A multiplexer chooses one many input signals and sends it to the output based on control signals.

Q9. What are the basic logic gates and their truth tables.

Ans 1: ANDGATE: Outputs 1 when all inputs are 1
OR GATE: Return 1 if at least one input is 1
NOT GATE: Returns the complement of the input.
These basic gates serve as the foundation for NAND, NOR, XOR, and XNOR gates.

Q10. Define Analog Signals

Ans 1: Analog signals are signals that change with time smoothly and continuously over time. They can have any value within a given range. Examples include voice signals, body's temperature, and radio wave signals.
